
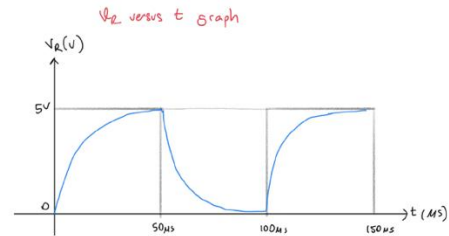


EXPERIMENT 5 – ONLINE VERSION FIRST ORDER CIRCUITS

Preliminary Work:

1.

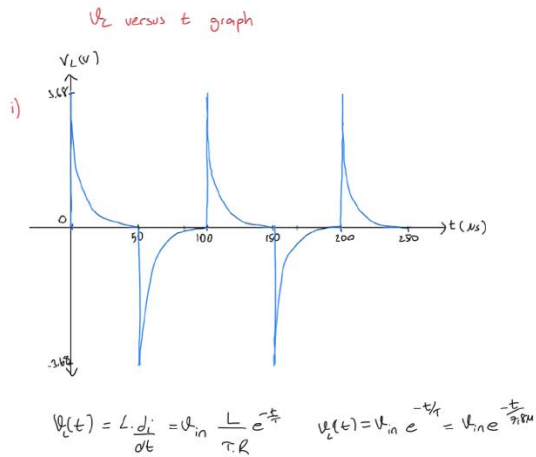

$$V_R(t) = i(t) \cdot R$$

$$= \frac{V_{in}(t)}{R} (1 - e^{-\frac{t}{\tau}}) \cdot R = V_{in}(t) (1 - e^{-\frac{t}{\tau}}) \quad \text{when } V_{in} = 0$$

ii) $\tau = \frac{L}{R} = \frac{39 \cdot 10^{-4}}{500} \quad \tau = 7.8 \mu s$

2.



case 1)

$$V_C(t) = \frac{1}{(3.3k) \cdot (4.7n)} \int_0^t V_{in}(t) dt$$

$$= \frac{1}{(1.551) \cdot (10^{-5})} \int_0^t V_{in}(t) dt$$

$$V_R(t) = (3.3k) (4.7n) \frac{dV_{in}(t)}{dt}$$
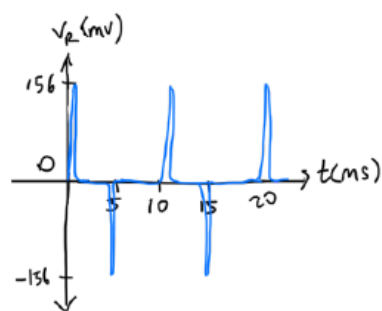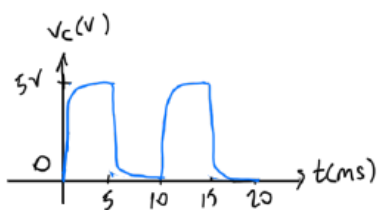
$$= (1.551) (10^{-5}) \frac{dV_{in}(t)}{dt}$$




$\tau = (3.3k) \cdot (4.7n) = 15.51 \mu s$

case 2)


$$V_C(t) = \frac{1}{(33k)(10n)} \int_0^t V_{in}(t) dt$$
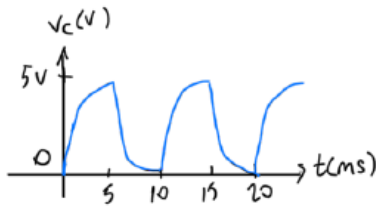
$$= \frac{1}{(3,3)(10^{-4})} \int_0^t V_{in}(t) dt$$



$$V_R(t) = (33k)(10n) \frac{dV_{in}(t)}{dt}$$
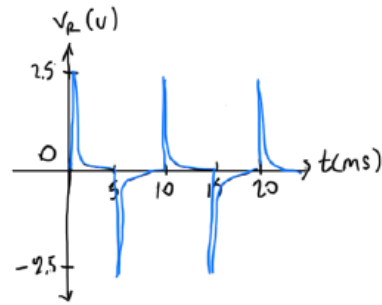
$$= (3,3)(10^{-4}) \frac{dV_{in}(t)}{dt}$$




$$T = (33k)(10n) = 330\mu s$$

case 3)


$$V_C(t) = \frac{1}{(33k)(47n)} \int_0^t V_{in}(t) dt$$
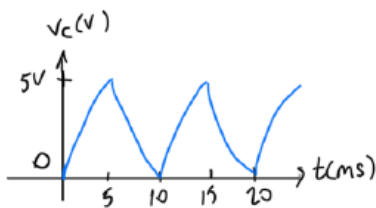
$$= \frac{1}{(1,551)(10^{-3})} \int_0^t V_{in}(t) dt$$



$$V_R(t) = (33k)(47n) \frac{dV_{in}(t)}{dt}$$
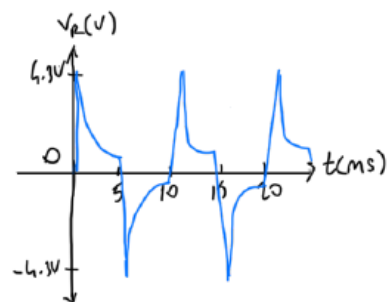
$$= (1,551)(10^{-3}) \frac{dV_{in}(t)}{dt}$$




$$T = (33k)(47n) = 1,551 ms$$

case 4)


$$V_c(t) = \frac{1}{(100k)(47n)} \int_0^t V_{in}(t) dt$$
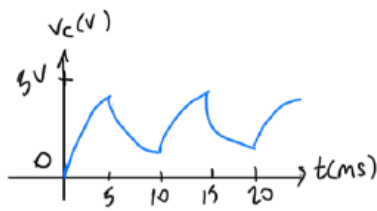
$$= \frac{1}{(4.7)(10^{-3})} \int_0^t V_{in}(t) dt$$



$$V_R(t) = (100k)(47n) \frac{dV_{in}(t)}{dt}$$
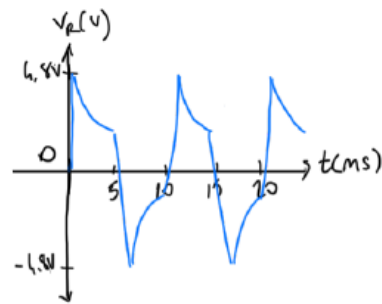
$$= (4.7)(10^{-3}) \frac{dV_{in}(t)}{dt}$$



$$T = (100k)(47n) = 4.7 \text{ ms}$$

3. If we choose time as τ (exponent of the e will be -1 , since in all equations e in the form of $e^{(-t/\tau)}$), solve the equation, we get a voltage value. At the first period, if we look at the corresponding time of this voltage we can find τ from graph. (for the 1st question)
For second question, since the given input is seen on the capacitor with exponential, then $t = \tau$, exponential is equal to 0.68 times of the V_{in} , so the corresponding time of this voltage we can find τ from graph.

EXPERIMENT 5 REPORT SHEET

Name :

Derya TINMAZ

Date : 31.12.2020

Experimental Work : 5

1)

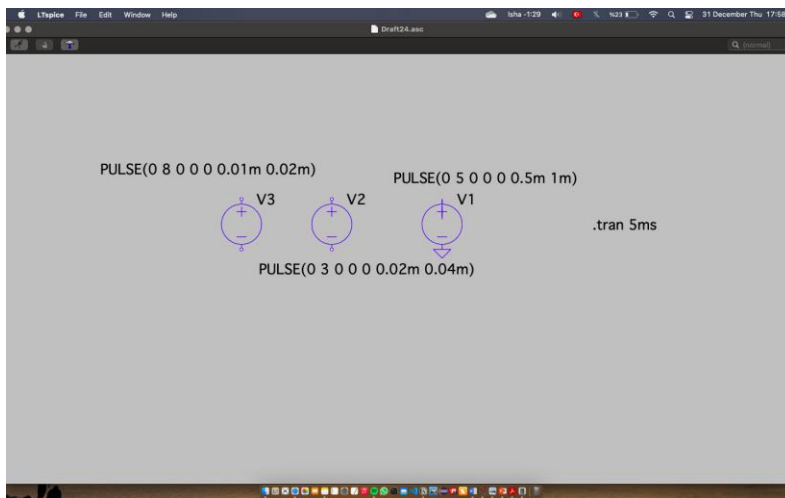


Figure 1: the image of the schematic of square wave sources

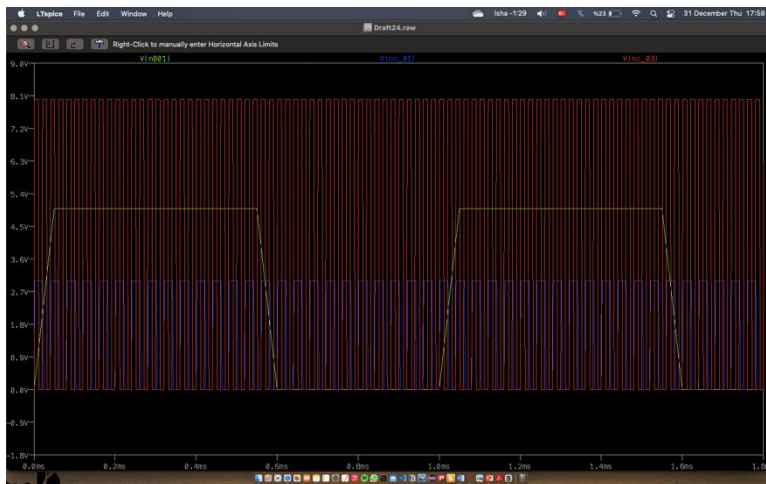


Figure 2: all the signals in a single scope output

Comments: The signal with greastest frequency has the smallest period, and its waves are closer to each other than other waves.

2.

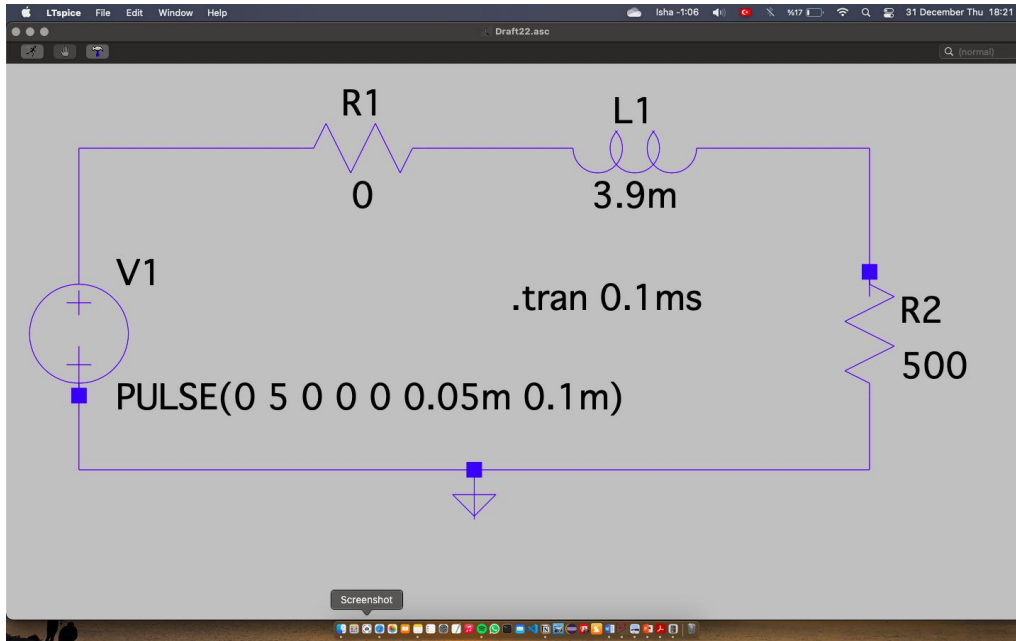


Figure 3: The schematic of the circuit in Figure 1a


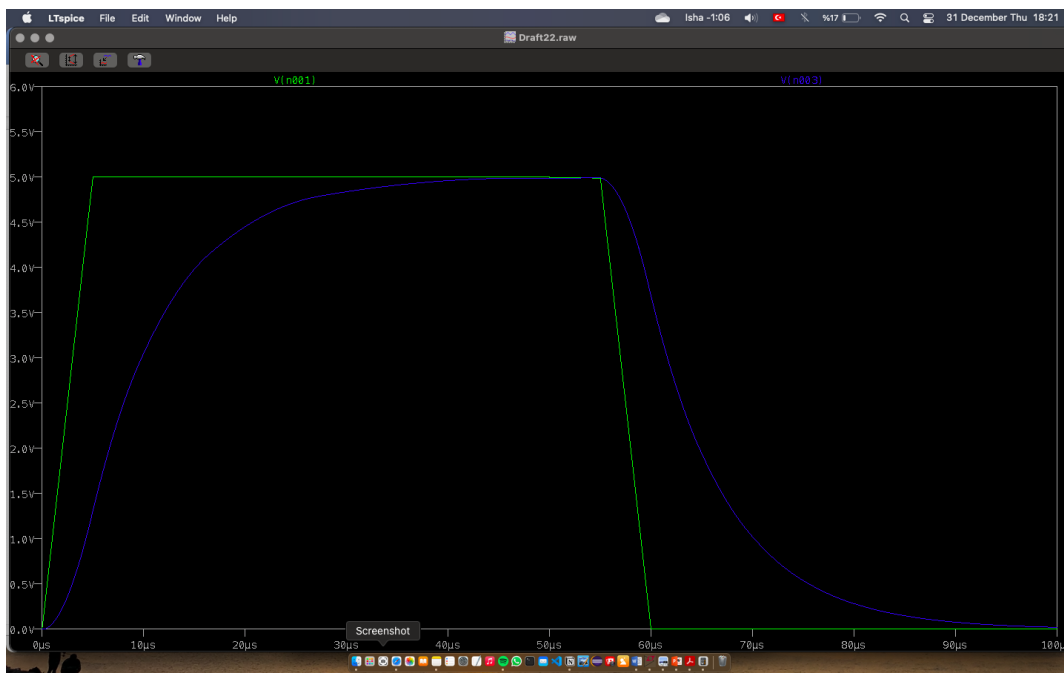


Figure 4: The scope output of the circuit($V_{in}(t)$ and $V_R(t)$)

Time constant τ :

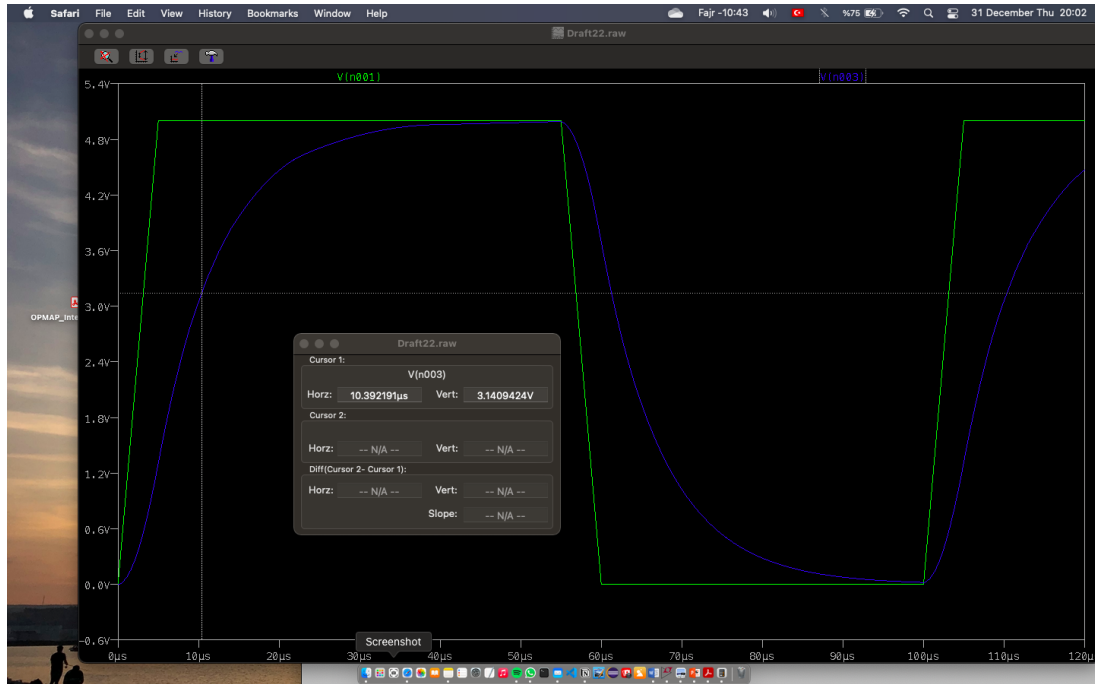

to find τ in the $V_R(t)$ graph:

$$V_R(t) = V_{in}(t) (1 - e^{-\frac{t}{\tau}})$$

$$\begin{aligned} \text{when } t = \tau &= V_{in}(t) (1 - e^{-1}) \\ &= V_{in}(t) (0.632) \\ \text{between } (50\mu s - 0) &= 5 \cdot 0.632 = 3.16 \end{aligned} \quad \left. \begin{array}{l} \text{so when } V = 3.16 \\ \text{the time is } \tau \\ \text{which is } 10.4\mu s \end{array} \right\}$$

Comments: The results are same as expected, just little differences due to floating point precisions.

3.

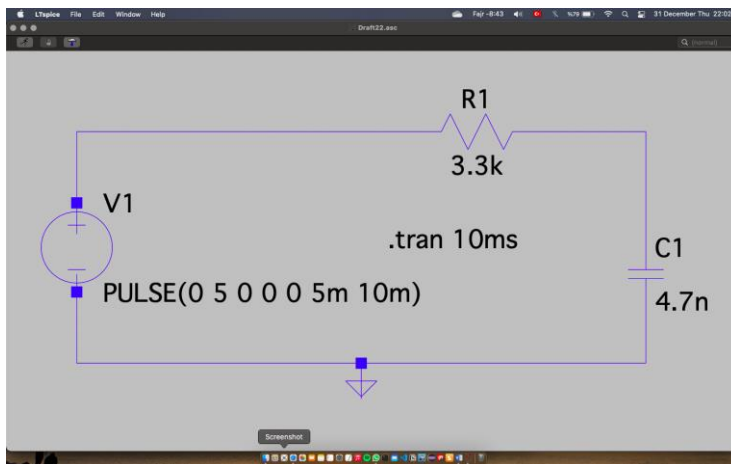


Figure 5: The schematic of the circuit in Figure 1b with case 1.

Case 1: $f=100\text{Hz}$, $R=3.3\text{k}\Omega$, $C = 4.7$

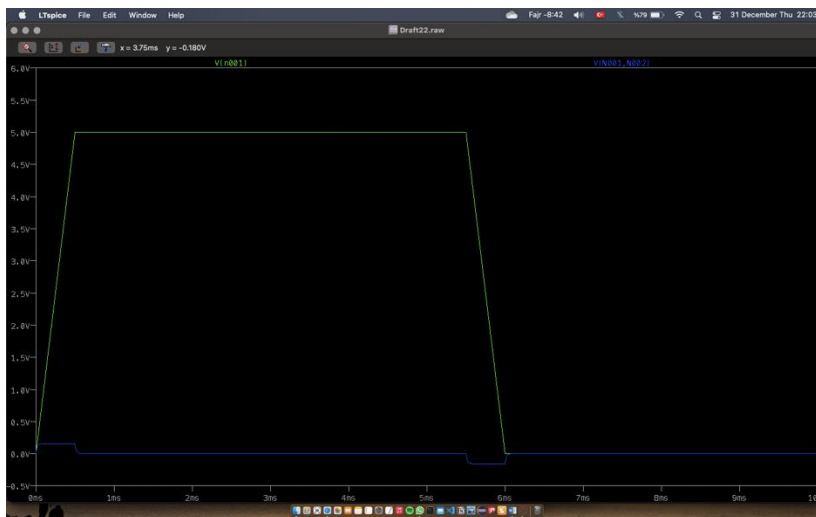


Figure 6: The scope output of the circuit($V_{in}(t)$ and $V_R(t)$)


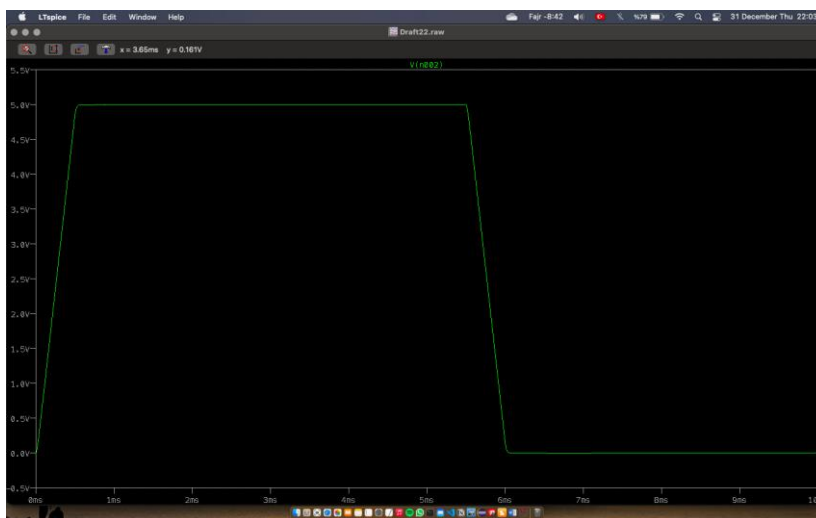


Figure 7: The scope output for $V_C(t)$

Time constant τ :

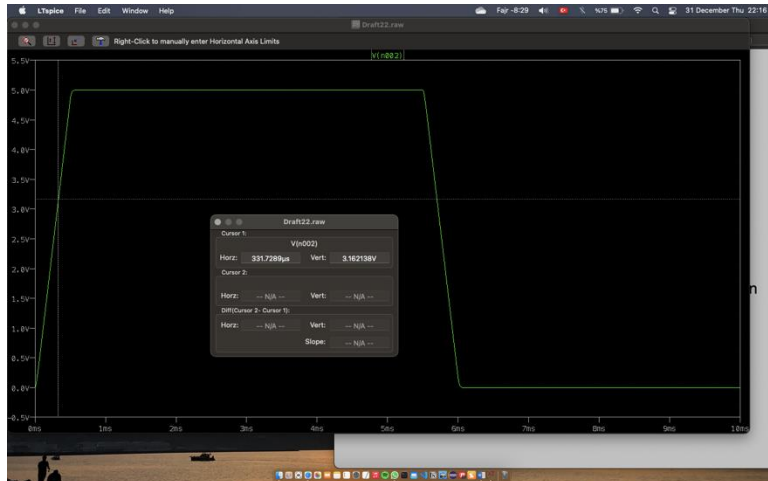

when $V_C(t) = 0.63 V_C$
 $= 0.63 \cdot 5 = 3.15$
 if we look corresponding time when $V_C = 3.15$ we get τ which is
 331,7 μ s.

Comments: The results are same as expected, just little differences due to floating point precisions.

Case 2: $f=100\text{Hz}$, $R=33\text{k}\Omega$, $C = 10 \text{ nF}$

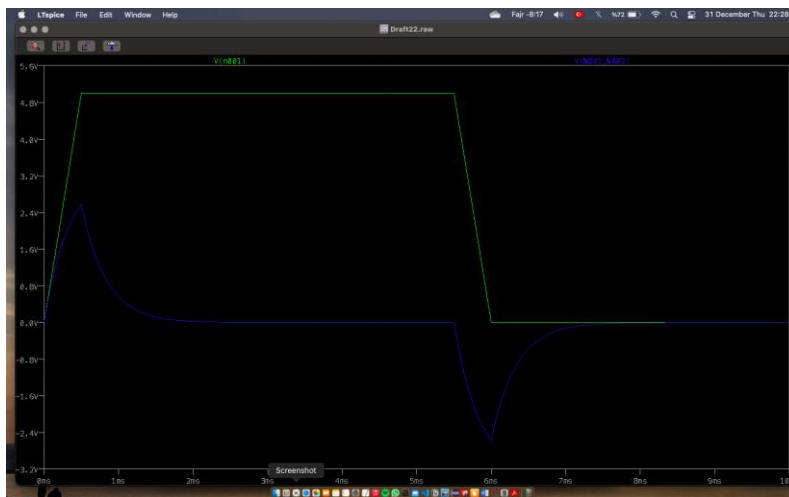


Figure 8: The scope output of the circuit ($V_{in}(t)$ and $V_R(t)$)


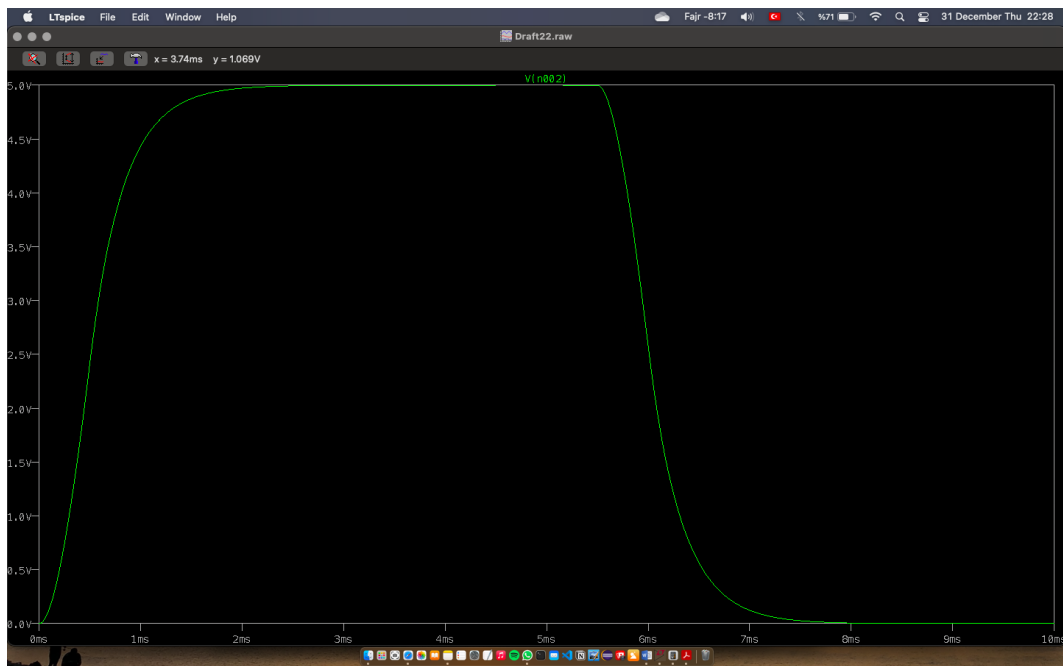


Figure 9: The scope output for $V_c(t)$

Time constant τ :

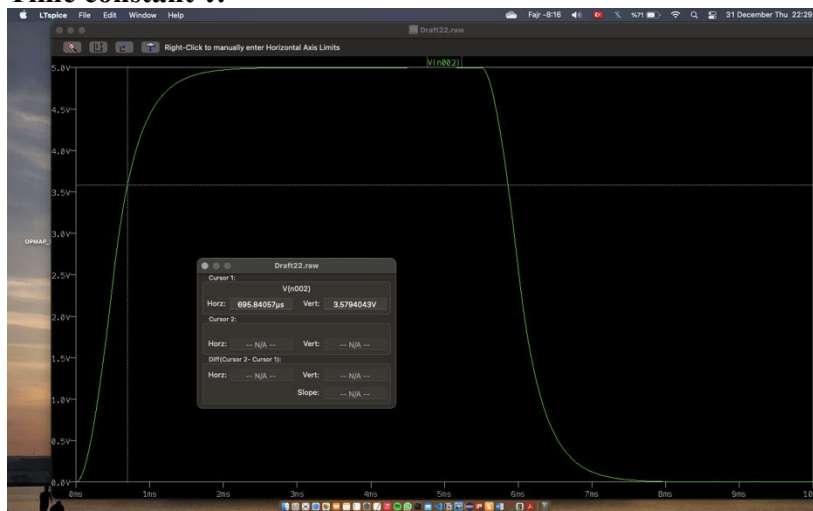

when $V_c(t) = 0.63V_c$
 $= 0.63 \cdot 5 = 3.15$
 if we look corresponding time when $V_c = 3.15$ we get τ which is
 $695.8 \mu s$.

Comments: The results are same as expected, just little differences due to floating point precisions.

Case 3: $f=100\text{Hz}$, $R=33\text{k}\Omega$, $C = 47\text{ nF}$

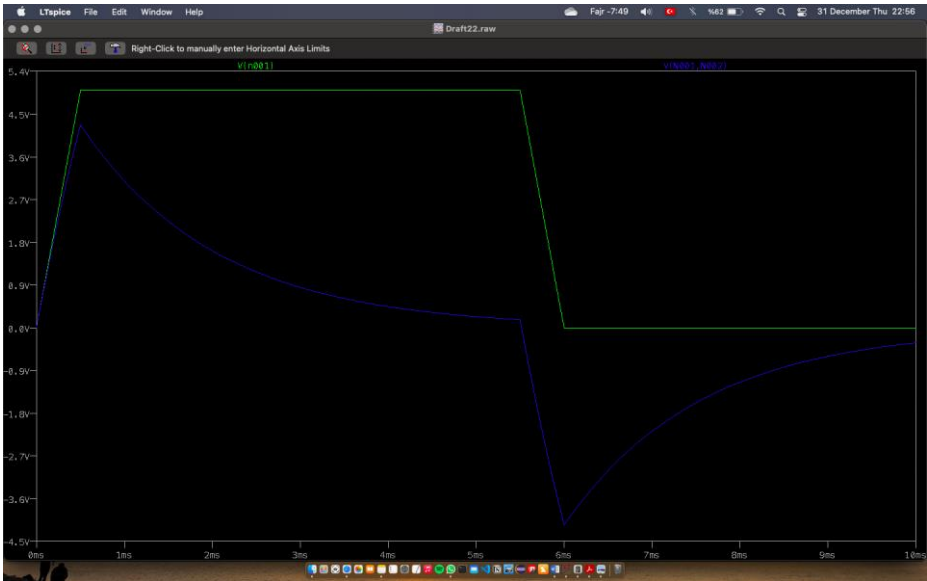


Figure 10: The scope output of the circuit($V_{in}(t)$ and $V_R(t)$)


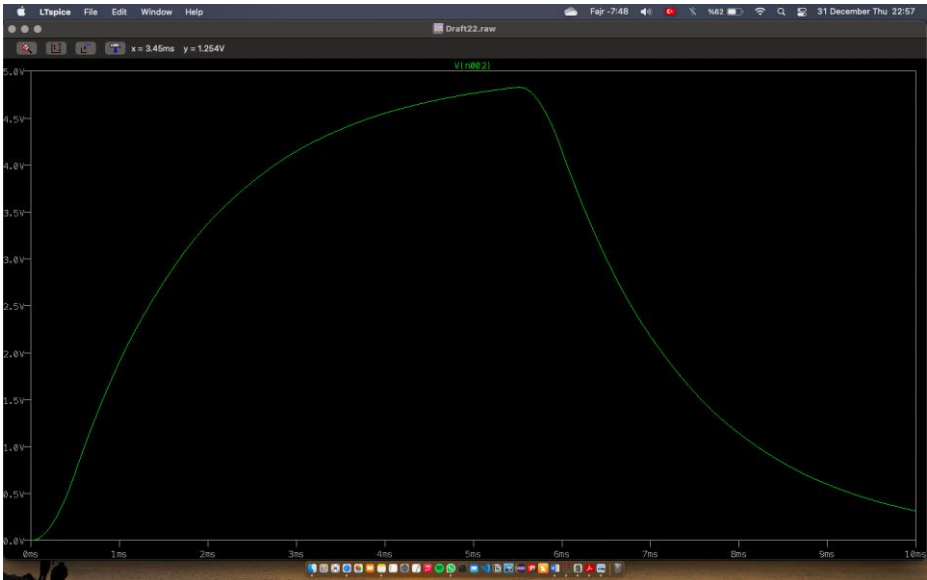


Figure 11: The scope output for $V_C(t)$

Time constant τ :

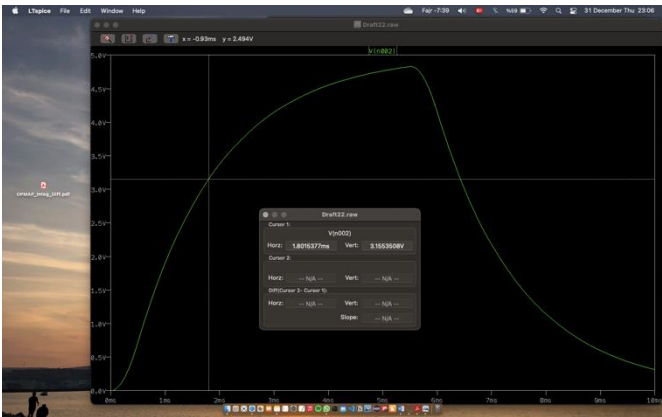

when $V_c(t) = 0.63 V_c$
 $= 0.63 \cdot 5 = 3.15$
 if we look corresponding time when $V_c = 3.15$ we get τ which is
 1.8 ms

Comments: The results are same as expected, just little differences due to floating point precisions.

Case 4: $f=100\text{Hz}$, $R=100\text{k}\Omega$, $C = 47 \text{ nF}$

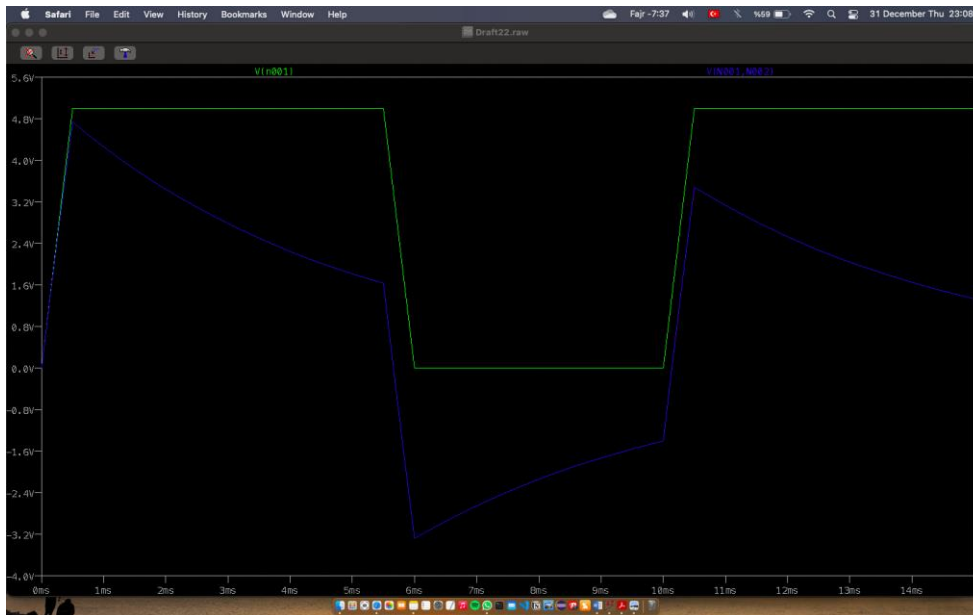


Figure 12: The scope output of the circuit($V_{in}(t)$ and $V_R(t)$)


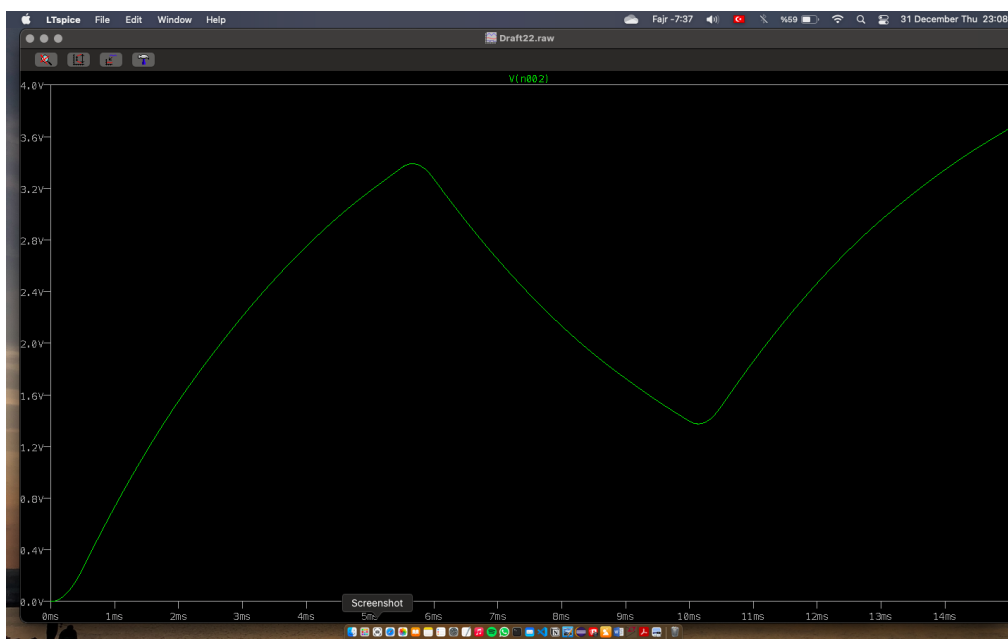


Figure 13: The scope output for $V_c(t)$

Time constant τ :

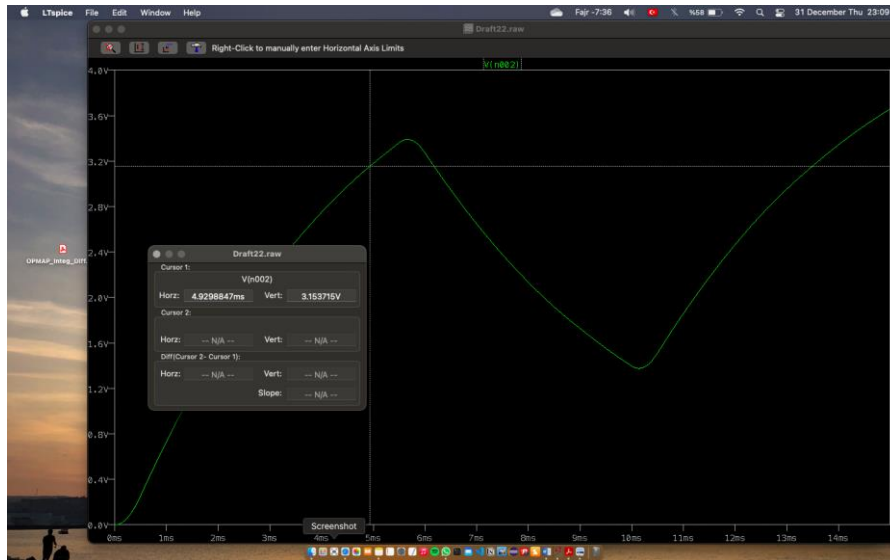

when $V_c(t) = 0.63 V_c$
 $= 0.63 \cdot 5 = 3.15$
if we look corresponding time when $V_c = 3.15$ we get τ which is
4.92ms

Comments: The results are same as expected, just little differences due to floating point precisions.