

8 - registers and counters

register


group of flip-flops
each storing one bit of information



• registers are used as temporary storage in a processor → faster than main memory

register with parallel load =

load=1 → we load the data

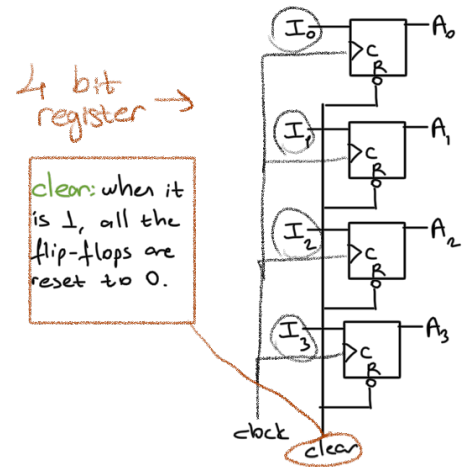load=0 → register content does not change



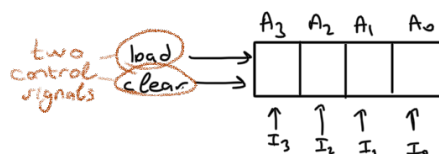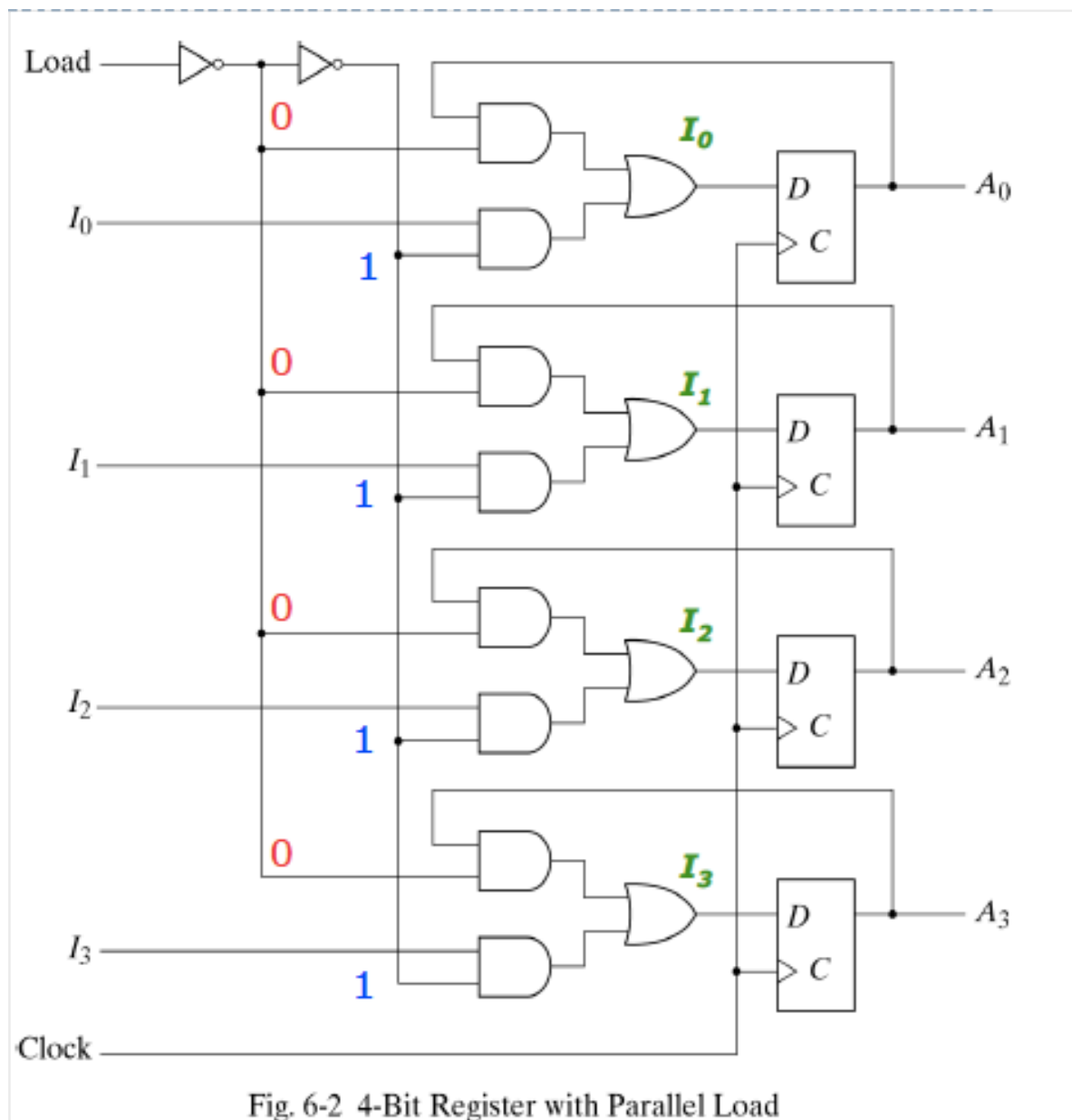


load=1 → register will receive data
clear=1 → register will be cleared to all 0

- register can act as the memory component of the sequential circuit


parallel registers = the input is loaded to the register in a single clock cycle
the number of bits that are loaded does not matter

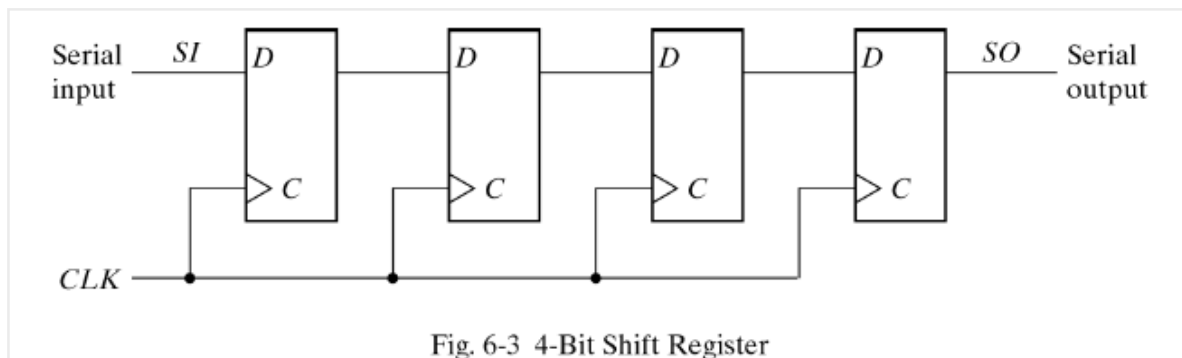shift (serial) registers = shifts its binary information in one or both direction




→ right shift register

loading 1100 to 1101 register:

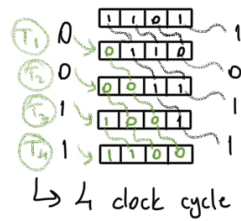


serial data transfer:

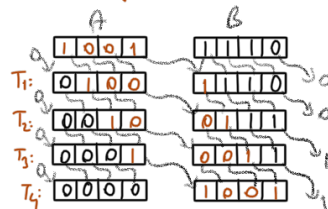


used in → keyboards, mice (input)
→ printers (output)
: USB or Firewire (data transfer)

parallel to serial / serial to parallel

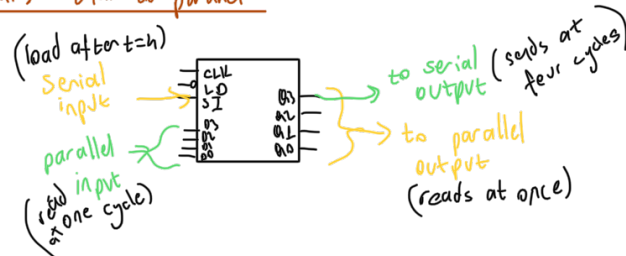

Universal Shift Register

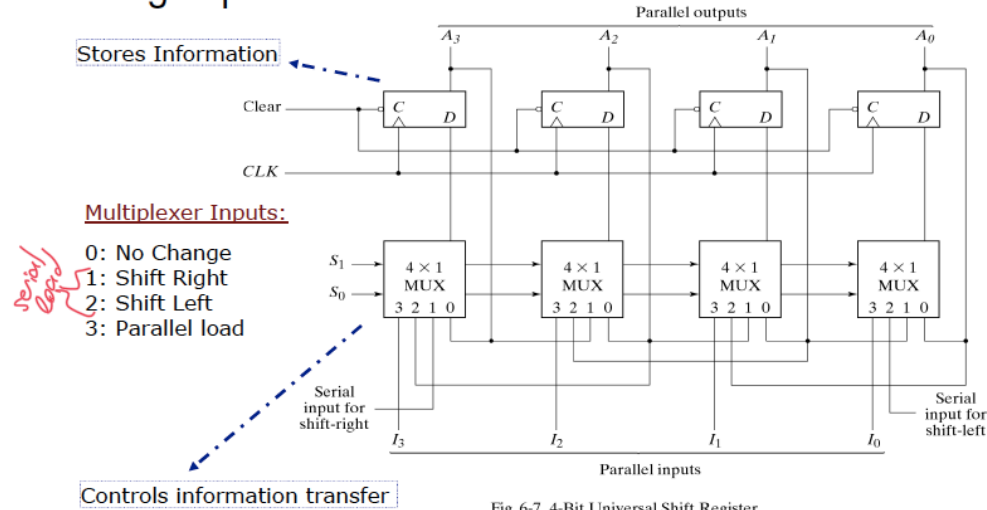- ▶ A register capable of shifting in both directions and loading in parallel.



parallel adder

n adders
one unit of time
(combinational circuit)

serial adder

one full adder
n units of time
(sequential circuit)

counters

a register that can go through a predetermined sequence of states (basically counts)
binary counter = counts through binary sequence, n bit counter counts from 0 to 2^n

counters

(wave)

ripple counters


the flip-flop output triggers other flip-flops in sequence

synchronous counters

count the clock

usage of counters:

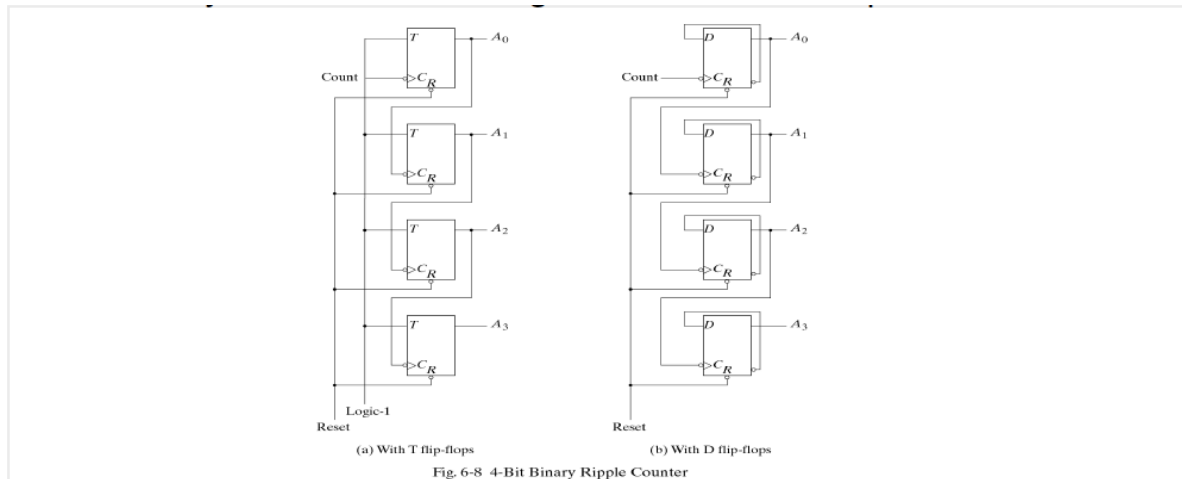- act as a simple clock → keep track of absolute/relative timing
- record how many times something has happened
- all processors contain a program counter, or PC → keeps track of instructions



binary ripple counter: consists of a series of complementing flip-flops, with the output of each flip-flop connected to the next higher order

*no clocks!

| A_3 | A_2 | A_1 | A_0 | |
|-------|-------|-------|-------|---|
| 0 | 0 | 0 | 1 | $\rightarrow A_0$ is complemented at each count pulse |
| 0 | 0 | 1 | 0 | $\rightarrow A_1$ is complemented when A_0 goes from 1 to 0 |
| 0 | 1 | 0 | 0 | $\rightarrow A_2$ is complemented when A_1 goes from 1 to 0 |
| 0 | 1 | 1 | 0 | $\rightarrow A_3$ is complemented when A_2 goes from 1 to 0 |
| 1 | 0 | 0 | 0 | |
| 1 | 0 | 0 | 1 | |

count-up counter


* in count-down counter, the bits change when previous bits go from 0 to 1

binary coded decimal \rightarrow

| | |
|----------------------|----------------------------|
| 0 \rightarrow 0000 | 10 \rightarrow 0001 0000 |
| 1 \rightarrow 0001 | 11 \rightarrow 0001 0001 |
| \vdots | \vdots |
| 9 \rightarrow 1001 | |

(down-count is complemented when all lower bits are 0)

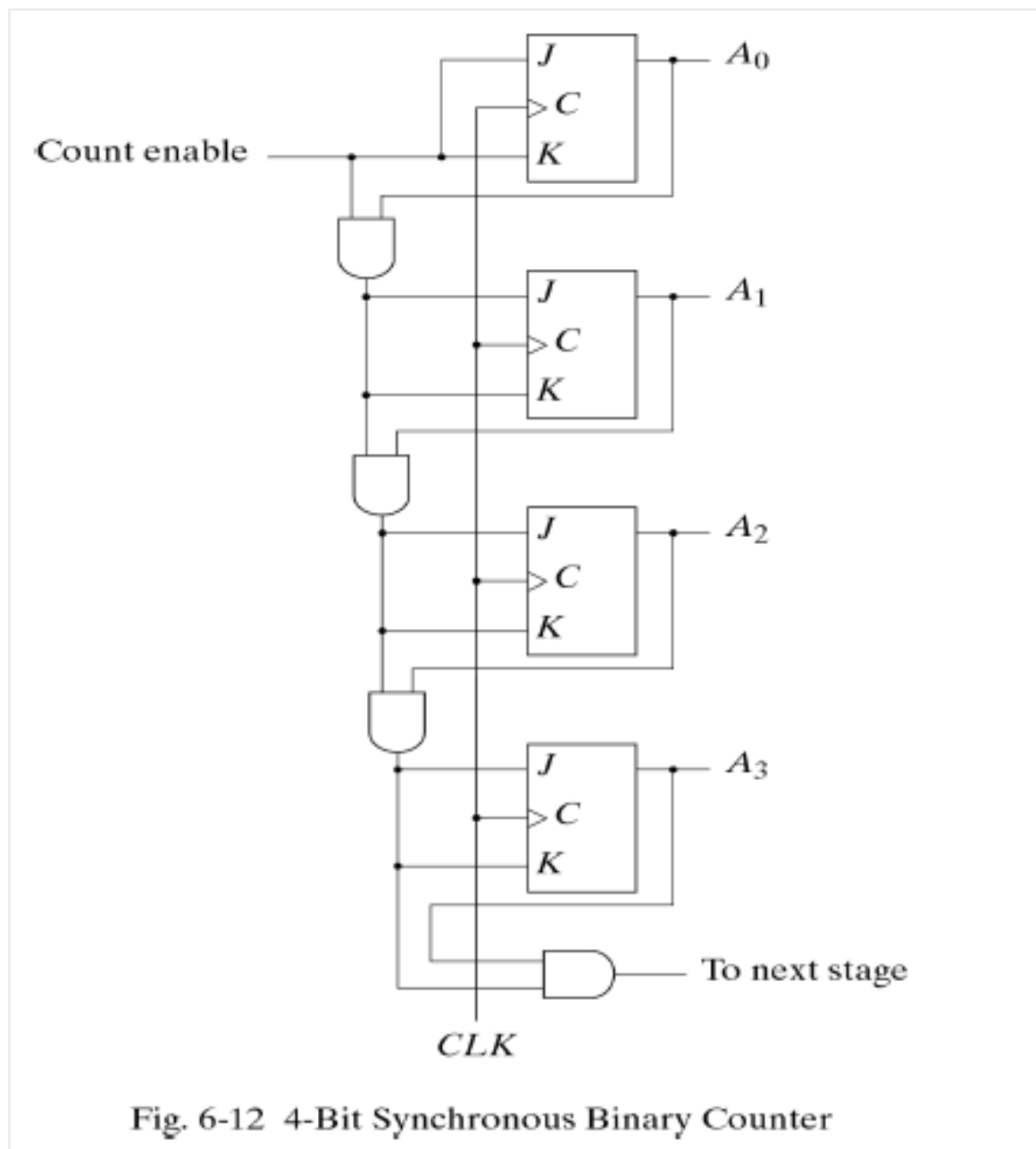Synchronous binary counter = when clock is 1 and all lower bits are one, it is complemented. (when $JK=11$ $Q \rightarrow Q'$)



☆ if we need initial value to count, we can add parallel load feature



other counters:

↳ ring counter:

| | | |
|------|---|------------------------------------|
| 0001 | } | counts only one flip-flop set to 1 |
| 0010 | | |
| 0100 | | |
| 1000 | | |

↳ johnson counter:

| | | |
|------|---|--|
| 0000 | } | they have same number of flip-flops (4) but, johnson can count twice more than ring. |
| 1000 | | |
| 1100 | | |
| 1110 | | |
| 1111 | | |
| 0111 | | |
| 0011 | | |
| 0001 | | |

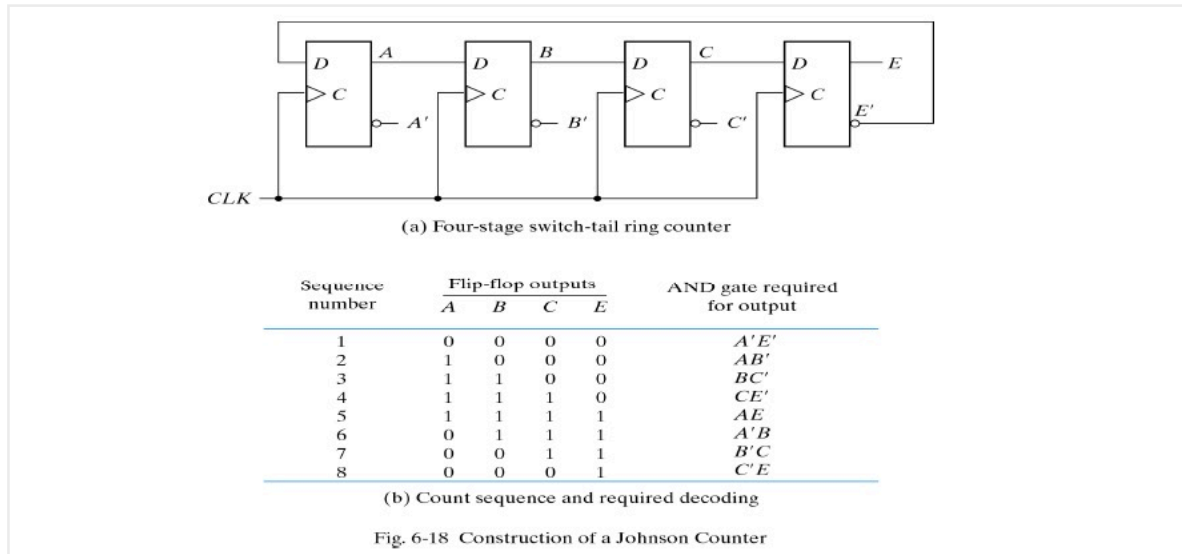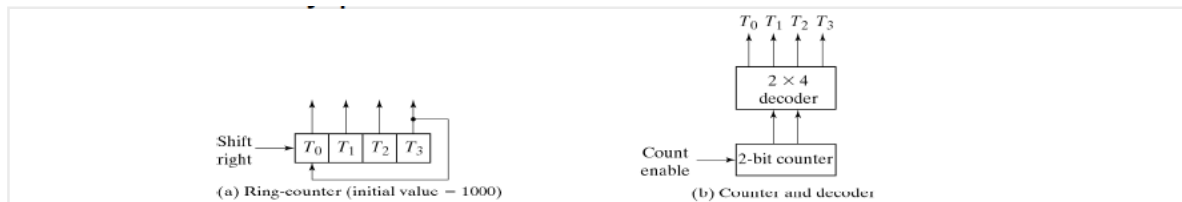

for ring counter:

| present | | | | next | | | | (D = Q _{next}) | | | |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|--------------------------|----------------|----------------|----------------|
| Q ₁ | Q ₂ | Q ₃ | Q ₄ | Q ₁ | Q ₂ | Q ₃ | Q ₄ | D ₁ | D ₂ | D ₃ | D ₄ |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |

$$D_3 = Q_1' \cdot Q_2 \cdot Q_3' \cdot Q_4'$$

synchronous = there is a clock, all change at the same time
asynchronous = no clock, they change in dependently of each other